
Application Manual

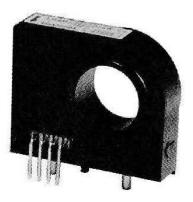

Overview


The L08P series comprises "through-type and onboard" current sensors of the open-loop type.

Characteristics

- · Single ±5V power supply.
- Through-type measured current.
- · Open-loop-type circuit configuration.
- · Onboard type
- $\cdot~$ Wide range of rated current, 100A \sim 300A.
- $\cdot\,$ The rated output voltage corresponding to the rated current is high (±4.0V), and high S/N ratio can be achieved.
- $\cdot\,\,$ The reference point of the output voltage is GND (0V).
- The offset voltage with respect to the rated output voltage is small ($\pm 0.75\%$).

Uses

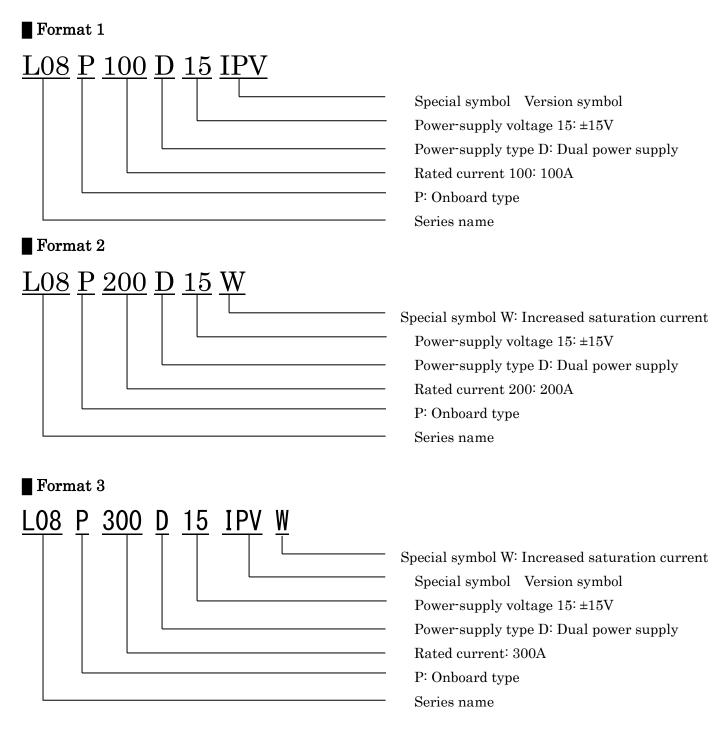- · General-purpose inverter
- \cdot Motor drive
- \cdot DCDC converter
- \cdot Generator
- \cdot UPS



Block diagram

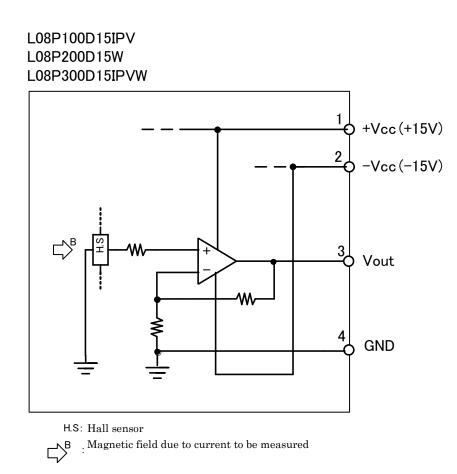



Fig. 1: Internal block diagram


Table 1: Description of terminals

Terminal	Terminal	Description	Remarks
number	name		
1	+Vcc	Plus power-supply terminal (+15V)	
2	-Vcc	Minus power-supply terminal (–15V)	
3	Vout	Output terminal	
		When the rated current If flows through the through hole,	
		the output voltage is 4.0V.	
		Standard load resistance: $10 \text{ k}\Omega$.	
4	GND	GND terminal	

Example of circuit <u>Standard circuit</u>

L08P100D15IPV L08P200D15W L08P300D15IPVW

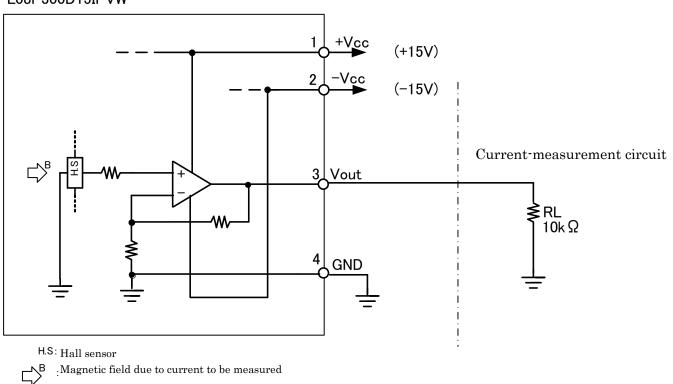

 

$\Box {\rm Description}$ of Fig. 2

This current sensor converts a measured current into a voltage. The output voltage Vout (3) in Fig. 2 is output on the basis of the GND voltage (Vref).

The relationship between Vout (3) and the current to be measured for each model number is shown in graphs 1 to 3 at the end of this document. Graphs 1 to 3 represent the standard values, and the effects of offset voltage, hysteresis errors, etc., are not included. The plus direction of the current to be measured is indicated by \rightarrow on the chassis (case or nameplate).

10 k Ω in Fig. 2 is the equivalent resistance of the receiving circuit of the current sensor output Vout (3). The load resistance between the Vout terminal (3) and the GND potential (0V) is used the standard value of 10 k Ω .

Circuit for setting the reference voltage to 2.5V

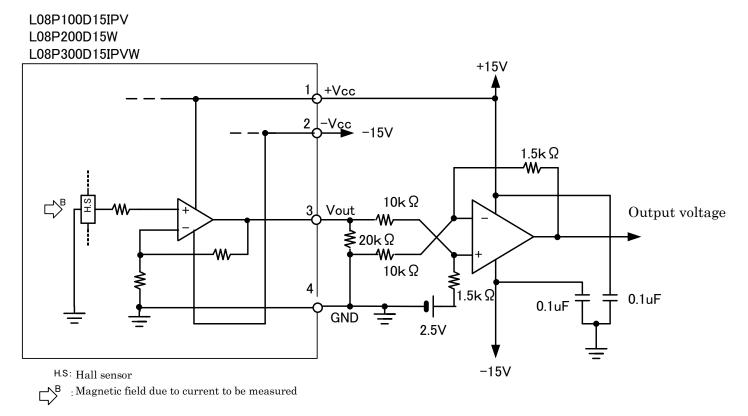


Fig. 3: Circuit for setting the reference voltage to 2.5V

\Box Description of Fig. 3

In this example, the reference value of the output voltage of the current sensor is converted from GND (0V) to the "+2.5V reference". This circuit is to be used for converting the reference voltage of the receiving circuit of the current detection signal to +2.5V from GND. When the current to be measured is 0A, the output voltage is 2.5V. When the rated current is detected, the output voltage is 0.6V + 2.5V = 3.1V. On the other hand, if the rated current is detected in the minus direction, the output voltage becomes -0.6V + 2.5V = 1.9V.

The relationship between detected current and output voltage for each model number is shown in Graphs 4 to 6 at the end of this document.

Application circuit

Electric-power system +

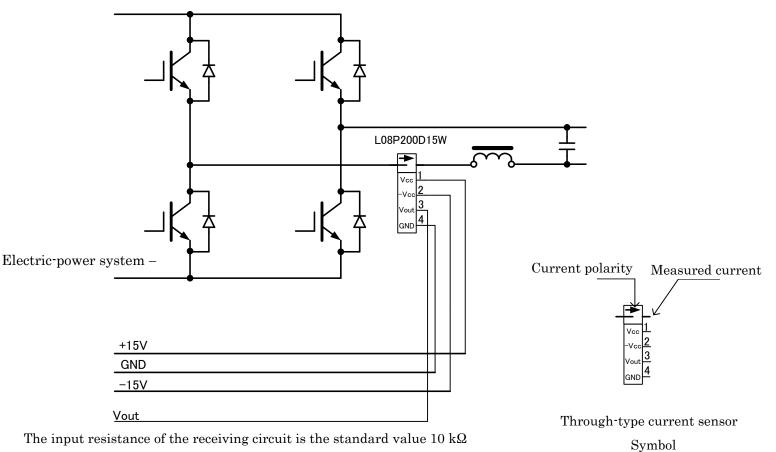



Fig. 4: Application to inverter circuits

■Implementation

Example of pattern design


Example of bus bar design



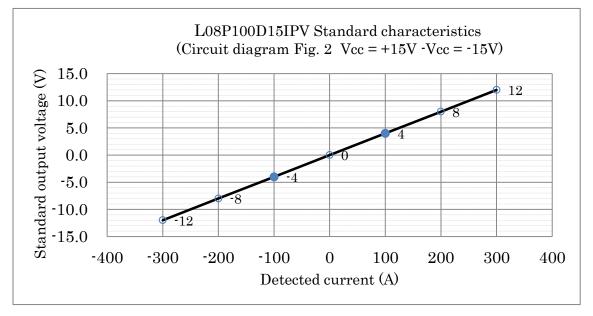


* •: The standard output voltage of the sensor versus the rated current.

 ${\rm Graph}\; 2$

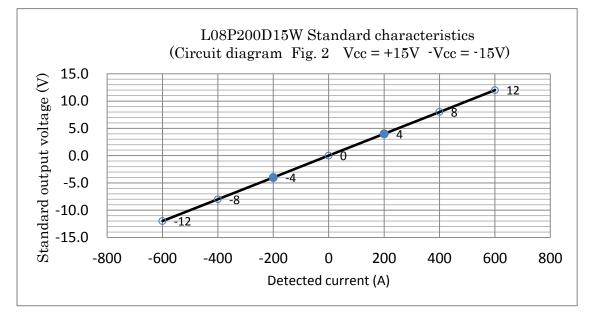

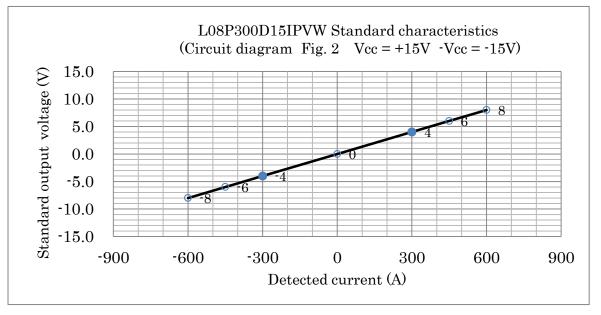
* •: The standard output voltage of the sensor versus the rated current.






* •: The standard output voltage of the sensor versus the rated current.

Graph 4

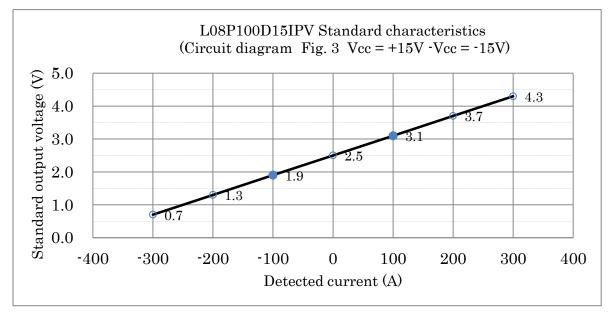

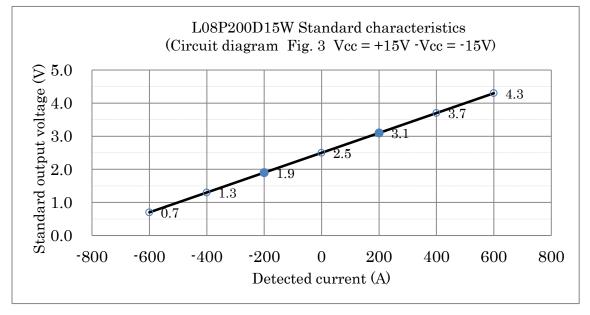* •: The standard output voltage of the sensor versus the rated current.





* •: The standard output voltage of the sensor versus the rated current.

Graph 6

